





Integrated Power Management with Switched-Capacitor DC-DC Converters

Hanh-Phuc Le, Michael Seeman, Vincent Ng., Mervin John
Prof. Seth Sanders and Prof. Elad Alon



UC Berkeley, California



Integration Challenges

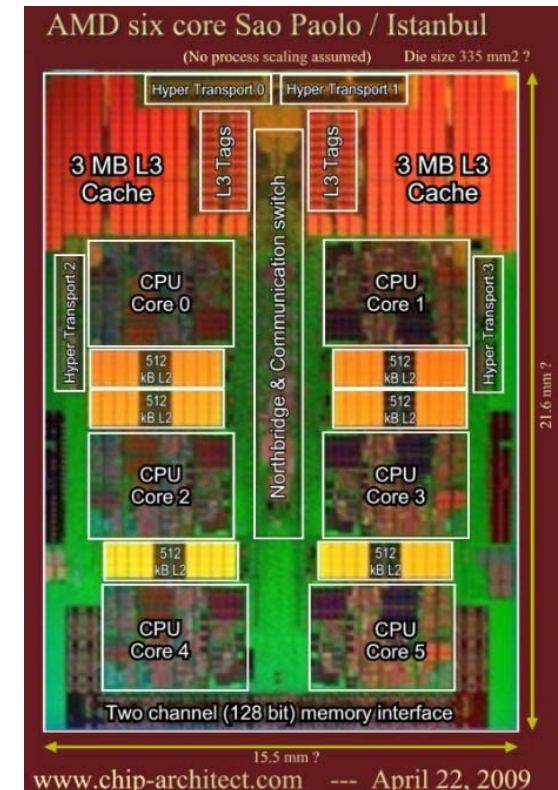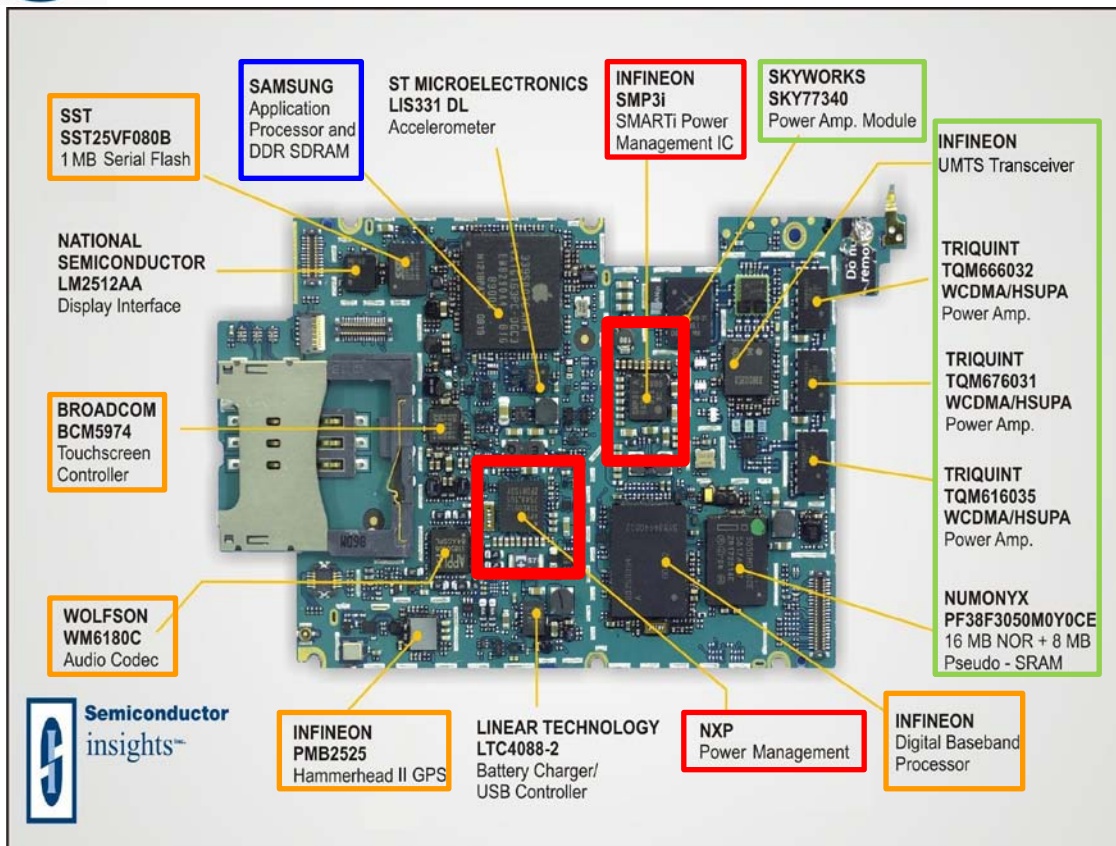

- **Integration has a benefit in energy efficiency**
 - Save IO power, board area
- **But it has a problem**
 - Need different voltage supply for different blocks/IPs and different modes of operations (DVS).




Limited Resources

  

Power pins

 
- Functions on-die increases the need for separate supply
- But the resources (pins and decap) are limited





Multiple Off-chip Supplies: Not Appealing

 
- Split power plane leads to supply impedance degradation
 - Compensating by de-cap is area-consuming → costly solution
- Just supplying power from off-chip is not appealing





Integrated DC-DC Converters

 - **One global supply onto die**
 - Local power generated by fully integrated DC-DC converters
- **Don't lose anything from package side**



→ How to make integrated DC-DC conversion efficiently?




Outline

- Motivation
- Integrated converter efficiency
 - Choice of energy storage element
 - Efficiency analysis
- Switched-capacitor converter design and prototype



DC-DC Converter: Linear vs. Switching


Linear Regulator

 

$$\eta = \frac{V_{out}}{V_{in}}$$

- Fundamental limit on efficiency

Switching Regulator

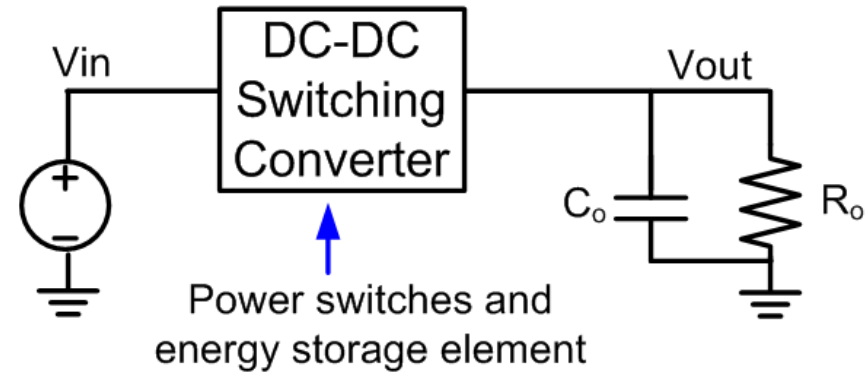


Inductor or Capacitor?

- Efficiency is ideally independent of conversion ratio.
- Theoretically, can reach up to 100% efficiency



SC – Operation of 2-to-1 Conversion


Phase 1

 

- Two-phase operation

- Phase 1: charge capacitor

Phase 2

 

- Phase 2: capacitor transfers charge to output


- Equivalent resistance from loss over switched-cap

$$R_{\text{switched-cap}} = \frac{1}{M_{\text{conv,cap}} f_{\text{sw}} C_{\text{fly}}}$$




Switched Capacitor Power Converters

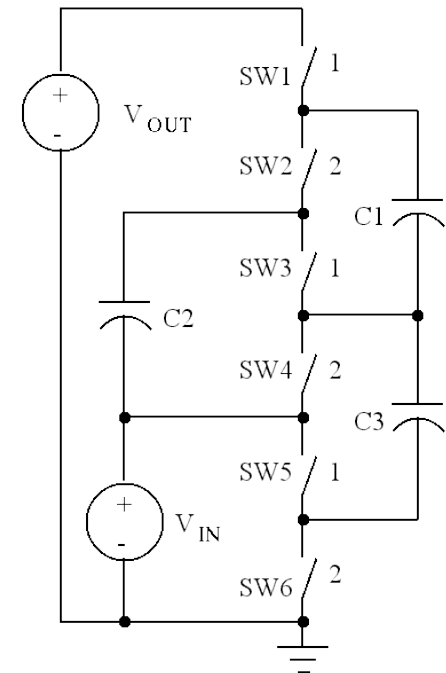- **Only switches and capacitors**
- **Using no inductors has advantages:**
 - Simplified full integration potential
 - Works well over a wide power range
 - Single mode, can adjust clock rate
 - No minimum load
 - No inductive switching losses
- **Open-loop loadline regulation possible:**
 - Output impedance has R-C characteristic, with R naturally designed to meet efficiency spec






First Look

 

Magnetic boost/buck:

 - 10-to-1 V conversion, 1A @ 1V
- S1,S2 rated for V-A product of $V \cdot I = 10 \text{ V-A}$
- Sum up to 20 V-A
- Need inductor, inductor loss,
- Inductive switching



10-to-1 Ladder Switched-Cap:

- 10-to-1 V conversion, 1A@1V
- 20 switches, each blocks 1V
- 18 switches handle $1/5 \text{ A}$
- 2 switches handle $9/5 \text{ A}$
- V-A product sums up to $36/5 = 7.2 \text{ V-A}$
- Intrinsic CMOS device convenient



The Submicron Opportunity

- **Rate device by ratio:** $G_s V_s^2 / C V_g^2$
 - Essentially an Ft type parameter for a power switch reflecting power gain
 - **Opportunity in scaling**
- **Suggests that we should look for opportunities to build our ckts with scaled CMOS based devices, but:**
 - Low voltage rating per device
 - Inadequate metal/interconnect for high current?





Why Not S-C ?

- Difficult regulation?
- Not suited for high current/power?
 - Magnetic-based ckts = higher performance?
- Interconnect difficulty for many caps?
- Voltage rating of CMOS processes?
- Ripple?




Previous Work

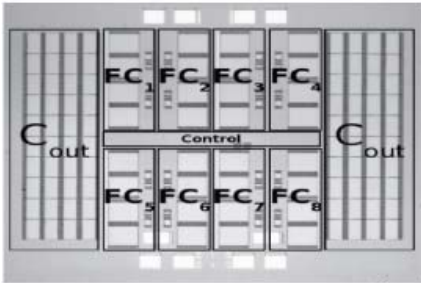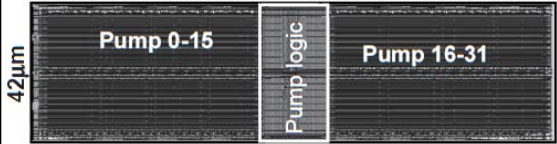Work	[1] Breussegem, VLSI 09	[2] Somasekhar, VLSI 09
Technology	130nm Bulk	32nm Bulk
Topology	2/1 step-up	2/1 step-up
Interleaved Phases	16	32
Converter Area (mm ²)	2.25	6.678x10 ⁻³
Power density @ η_{\max}	2.09 mW/mm ²	1.123 W/mm ²
Efficiency (η_{\max})	82%	60%
Die photo		



Switched Capacitor Loss



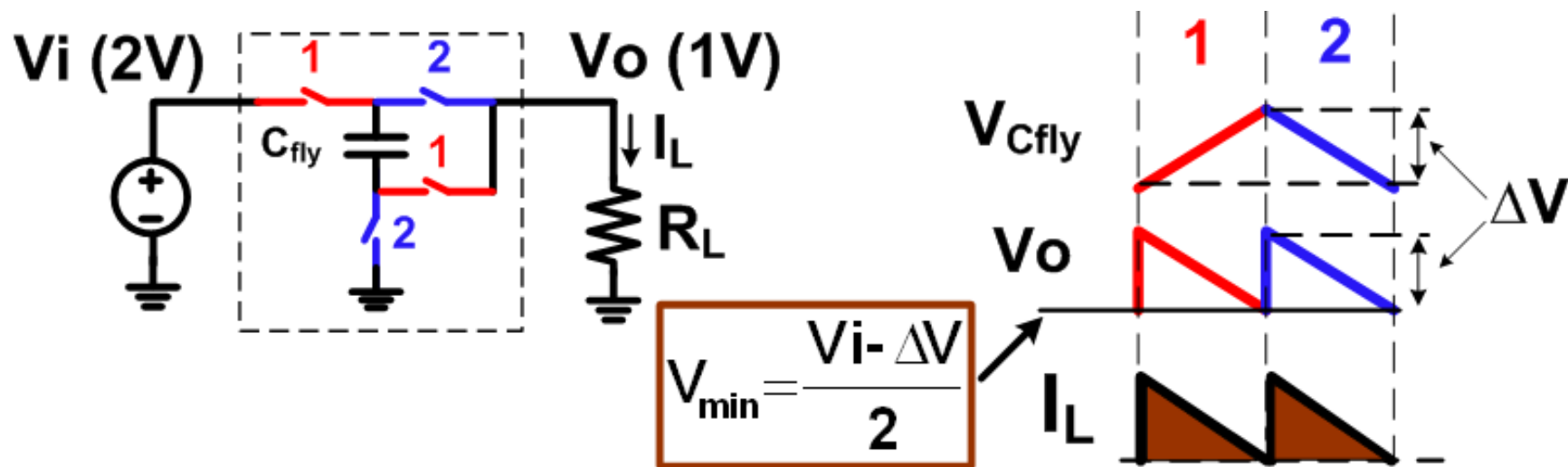


- Converter supplies digital circuits
 - Performance (f_{CPU}) set by V_{min}
- Intrinsic switched-capacitor loss:


$$P_{C_{fly}} = 2x \frac{I_L^2}{M_{conv,cap} f_{sw} C_{fly}}$$



Multi-Phase Interleaving

   

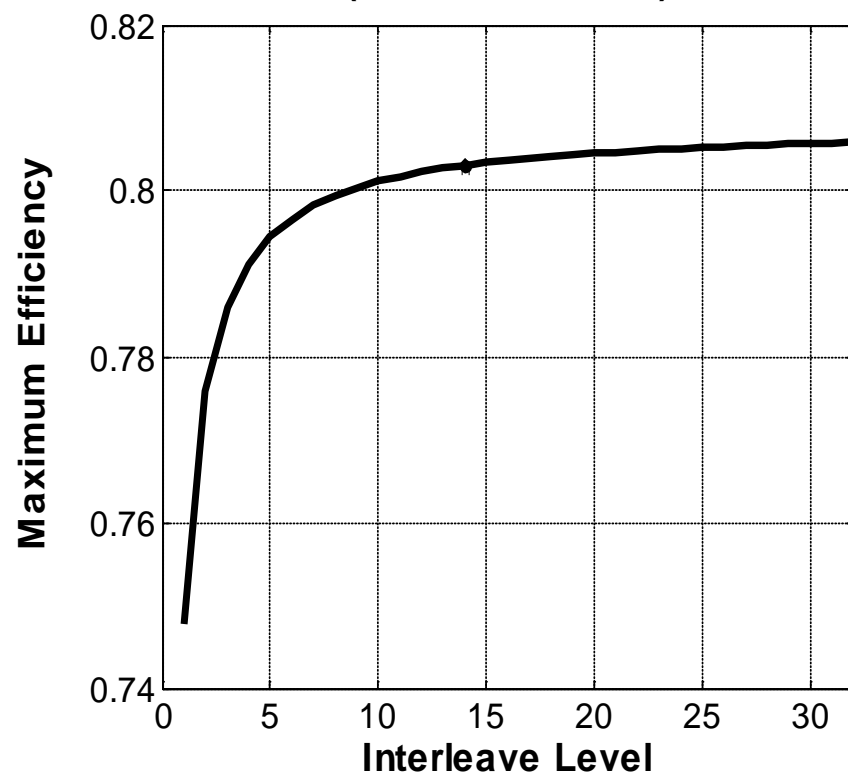Maximum Efficiency vs. Interleave
($V_{in}=2V$, $br=2.7\%$)





Good news:

- Interleaving can reduce ripple without changing V_{min}

$$P_{C_{fly}} = \left(1 + \frac{1}{k_{interleave}} \right) \frac{I_L^2}{M_{conv,cap} f_{sw} C_{fly}}$$



SC Analysis: Simplest Example

  

- **Slow Switching Limit (SSL):**

- Impulsive currents (charge transfers)
- Resistance negligible (assume $R = 0$)
- This (SSL) impedance is the switching loss!

$$i = f_{sw} \Delta q = \boxed{f_{sw} C \Delta v}$$

- **Fast Switching Limit (FSL):**



- Constant current through switches
- Model capacitors as voltage sources ($C \rightarrow \infty$)

$$i = \boxed{\frac{1}{4} \frac{1}{R}} \Delta v$$

$$(\Delta v = V_{IN} - V_{OUT})$$



SC – Loss Optimization

  

4 main loss components

$$P_{\text{loss}} = P_{R_{\text{sw}}} + P_{C_{\text{fly}}} + P_{\text{bott.cap}} + P_{\text{gate.cap}}$$

$$\propto I_L^2 \frac{R_{\text{on}}}{W_{\text{sw}}}$$

Switch resist.

$$\propto \frac{I_L^2}{f_{\text{sw}} C_{\text{fly}}}$$

Switched cap

$$\propto C_{\text{bott}} f_{\text{sw}}$$

Bottom Plate

$$\propto W_{\text{sw}} C_{\text{gate}} f_{\text{sw}}$$

Gate loss

Series Losses (R_o)

Parasitic Losses ($R_{//}$)




Optimization for Efficiency

$$P_{\text{loss}} = P_{\text{Rsw}} + P_{\text{Cfly}} + P_{\text{bott.cap}} + P_{\text{gate.cap}}$$

- No bottom plate cap, optimize switch sizes W_{sw} and switching frequency f_{sw}



$$\frac{P_{\text{loss}}}{P_{\text{Load}}} = 3M_{\text{conv,tech}} \sqrt[3]{\frac{V_{\text{sw}}^2 R_{\text{sw}} C_{\text{gate}}}{V_o^2 R_L C_{\text{fly}}}}$$

Efficiency vs. Cap. Density

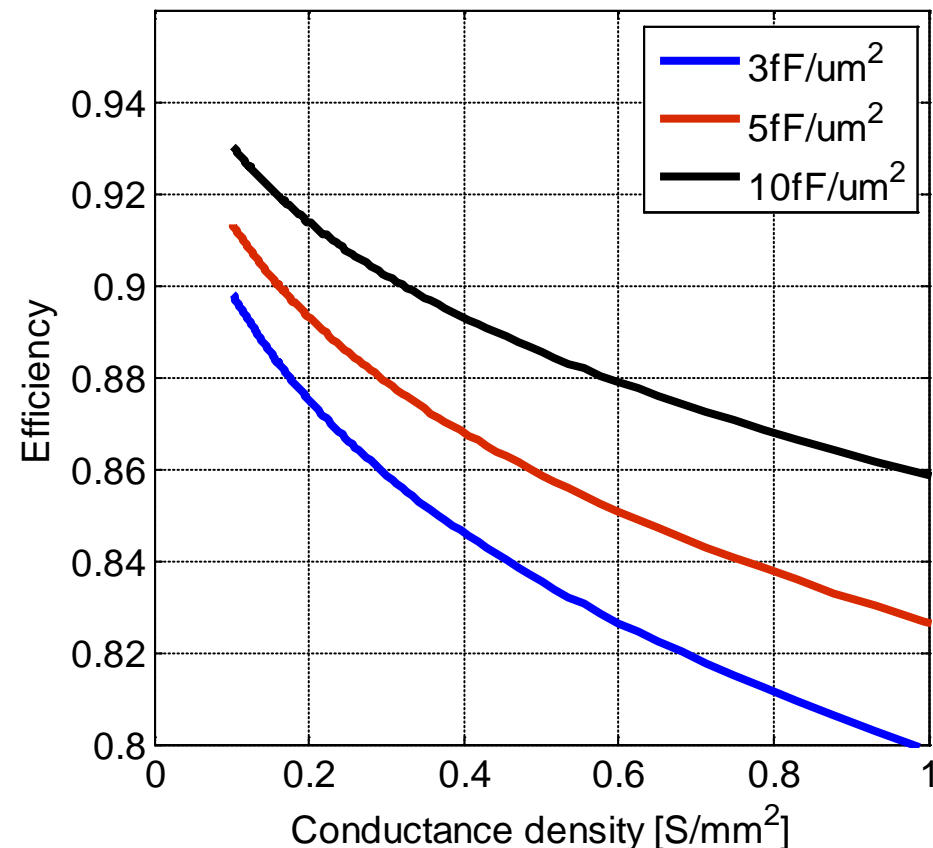



Optimization for Efficiency

 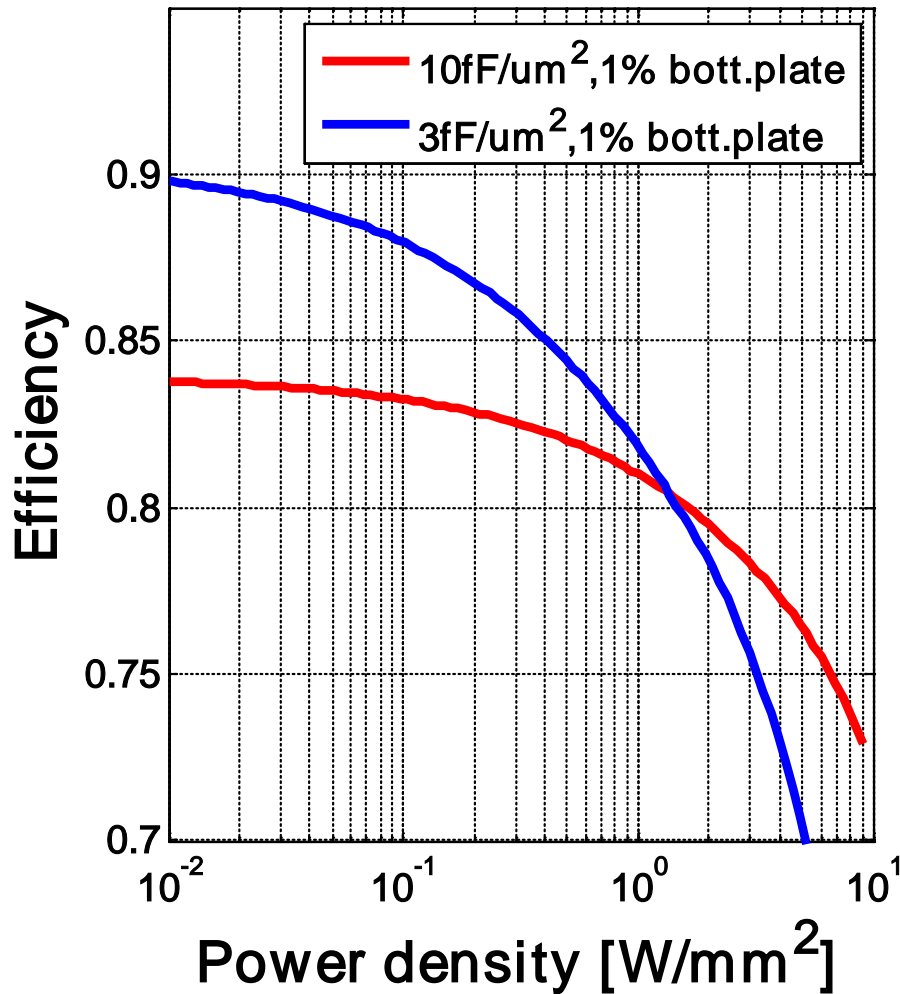

- **Efficiency and Power density trade-off**
- **At lower power density:**
 - Bottom plate critical
- **At high power density:**
 - Flying cap critical


$$\frac{P_{\text{loss}}}{P_{\text{Load}}} \approx \sqrt{M_{\text{conv}} k_{\text{bott}}} + \sqrt{\frac{1}{\sqrt{M_{\text{conv}} k_{\text{bott}}}}} \frac{V_{\text{sw}}^2 R_{\text{on}} C_{\text{sw}}}{V_o^2 R_L C_{\text{fly}}}$$



Achievable Performance

Eff. vs. Cap Density

($k_{\text{bott}} = 3\%$)

 

- **Looks promising**
 - Especially in mobile applications
 - 1W/mm² converter fits in decap area
- **Only looked at 2:1 converter so far**
 - Need to support multiple output voltage levels




Outline

- Motivation
- Integrated converter efficiency
 - Choice of energy storage element
 - Efficiency analysis
- Switched-capacitor converter design and prototype




Multiple Conversion Ratios


$n = 1/2$

 


$n = 2/3$

 


$n = 1/3$

 

 - Standard cell design supports multiple conversion ratios
- Fine output voltages achieved by controlling f_{sw} (or W_{sw})
 - Equivalent to linearly regulating down from peak efficiency
- How to drive the switches?





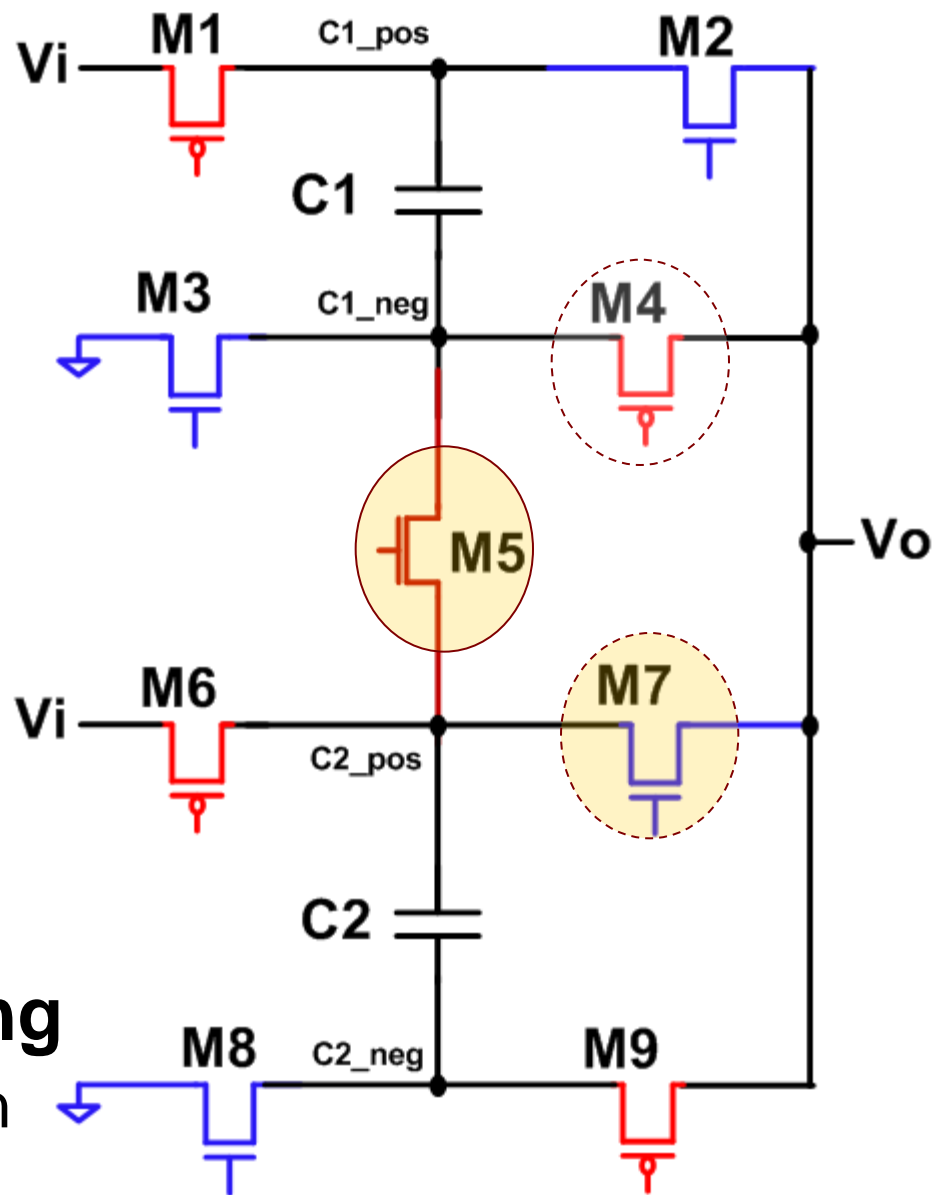


- p.23**



Switch Driver – M5

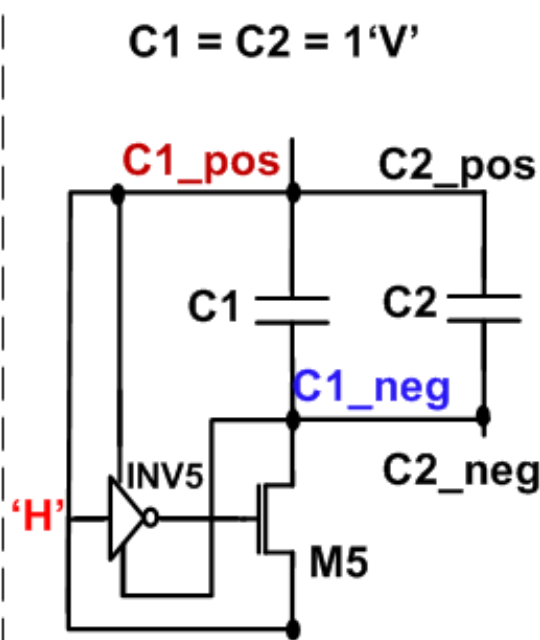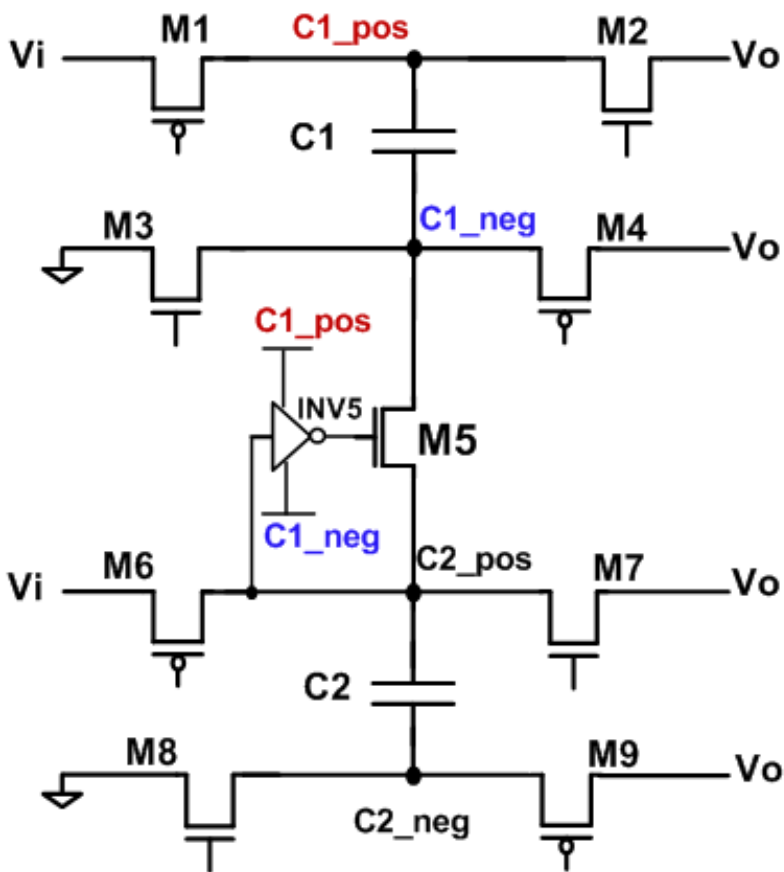

Caps in Parallel

 


Caps in Series




- “Flying” inverter INV5 powered off of C1
 - Controlled by top-plate of C2
- Automatically synchronized by operation of other switches



SC Converter Prototype


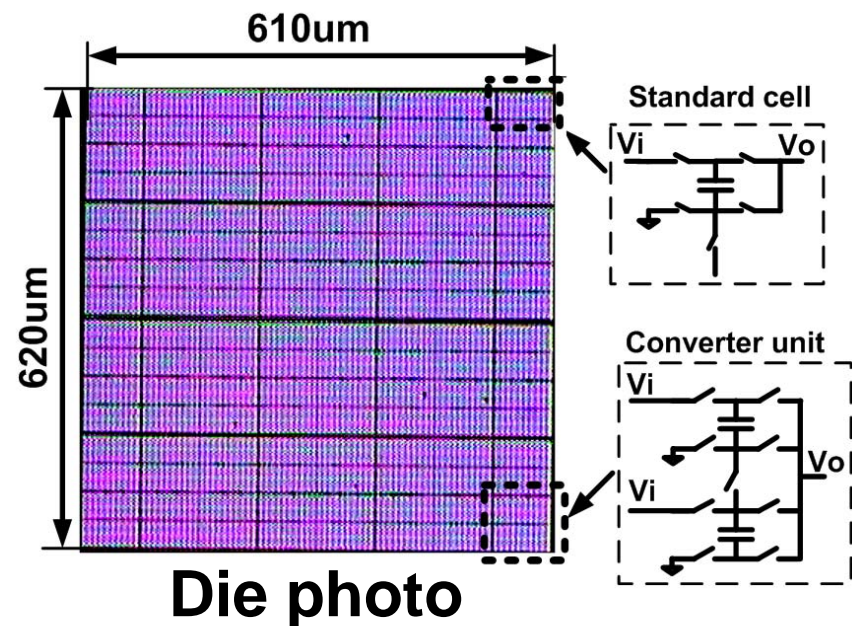


   - Implemented in 32nm SOI test-chip
- 32-way interleaved
- Supports 0.6V ~ 1.2V from 2V input






Measured Eff. vs. P-density

  


- Measured in 1/2 mode ($V_i = 2V$, $V_o \approx 0.88V$)
- Results promising: 81% efficiency @ 0.55 W/mm²



Measured Eff. vs. Topologies

 

Efficiency vs. V_o

 

f_{sw} vs. V_o

Settings:

$V_i = 2V$

$R_L \approx 4\Omega$ at


$V_o = 0.8V$.



How to get 10W/mm²?


- If 10W/mm² possible,
 - Converters will fit in decap of high performance processors
- What does it take to get there?
 - Effective cap density:
 - 30~50fF/um²
 - 3D packaging
 - New switch technology
 - MEMS
 - Others?
 
$$\frac{P_{loss}}{P_{Load}} = 3M_{conv,tech} \sqrt[3]{\frac{V_{sw}^2 R_{sw} C_{gate}}{V_o^2 R_L C_{fly}}}$$





Hybrid Regulator

 

▪ Separate control range

- Switched-cap converter controls low frequency (DC) impedance
- Linear regulator controls high frequency (AC) impedance
 - Only active when needed.

Ref: E. Alon and M. Horowitz, "Integrated Regulation for Energy-Efficient Digital Circuits," *IEEE J. Solid State Circuits*, vol. 43, no. 8, pp. 1795-1807, Aug. 2008.



Conclusions

- **Clear needs for fully-integrated DC-DC converters**
 - Switched-cap: a promising option
- **First demonstration achieves both high power density and high efficiency**
 - In 2:1: 81% efficiency at $0.55\text{W}/\text{mm}^2$
- **Reconfigurable to maintain efficiency over wide output voltage range**
 - $>70\%$ efficiency for V_o from $\sim 0.7\text{V}$ to 1.15V
- **Will need close-loop regulation and higher power density.**



Acknowledgement

- **AMD**
 - Layout team in India (Siddika Gundlur, Uttam Singhal)
 - Test team in Austin (Mike Bourland, Mike Jackson, Kevin Nguyen)
- **NSF Infrastructure Grant No. 0403427**
- **IFC**
- **BWRC Sponsors**
- **C2S2**